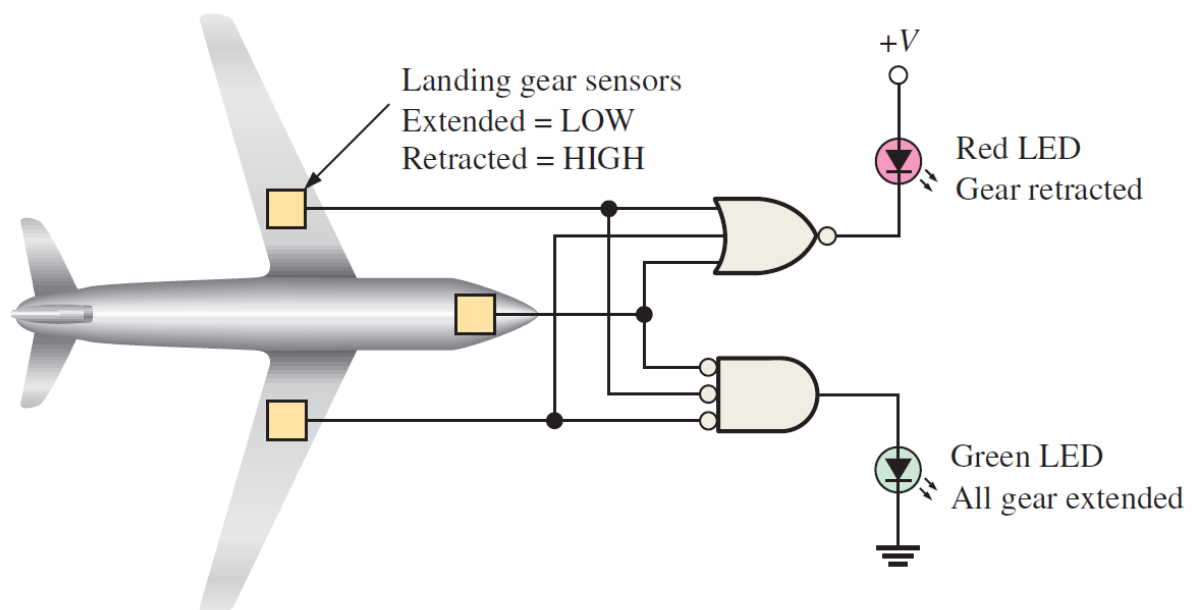


SI100EEE – Introduction to Information Science and Technology

Homework #1 Solution


Design Problem 1:

As part of an aircraft's functional monitoring system, a circuit is required to indicate the status of the landing gears prior to landing. A green LED display turns on if all three gears are properly extended when the "gear down" switch has been activated in preparation for landing. A red LED display turns on if any of the gears fail to extend properly prior to landing. When a landing gear is extended, its sensor produces a LOW voltage. When a landing gear is retracted, its sensor produces a HIGH voltage. Implement a circuit to meet this requirement.




Design Problem 2:

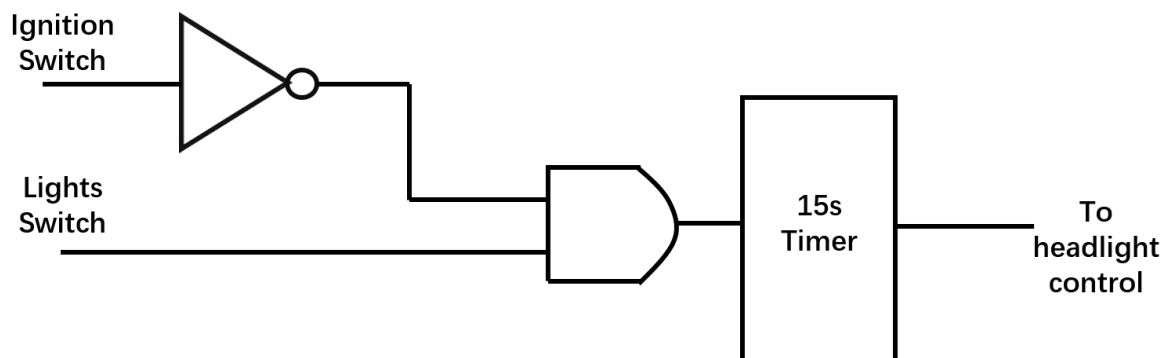Design a circuit to fit in the beige block of Figure 2 that will cause the headlights of an automobile to be turned off automatically 15 s after the ignition switch is turned off, if the light switch is left on. Assume that a LOW is required to turn the lights off.



Design Problem 3:

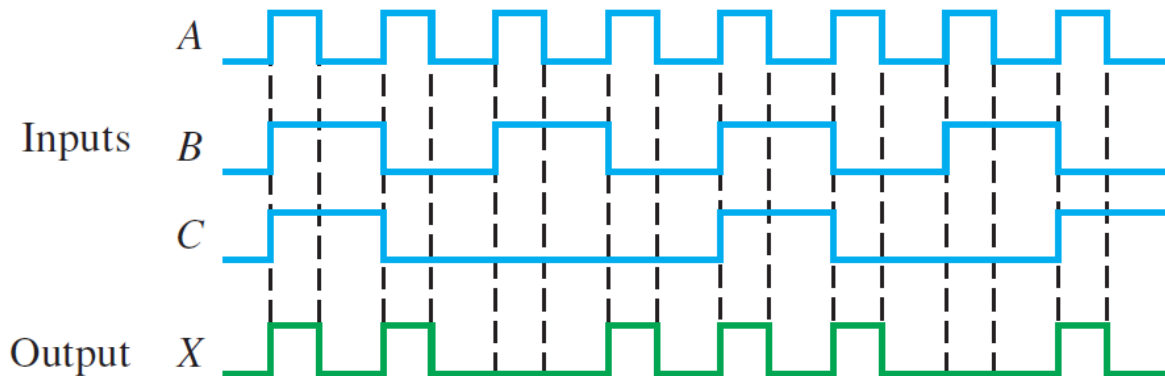Design a logic circuit so that it will generate the output waveform shown in Figure 3.



The corresponding truth table is

A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

$$X = A\bar{B}\bar{C} + AC$$