




Lecture 3B: Seven-Segment Display




Xufeng Kou
**School of Information Science and
Technology**
ShanghaiTech University



Seven Segment Display

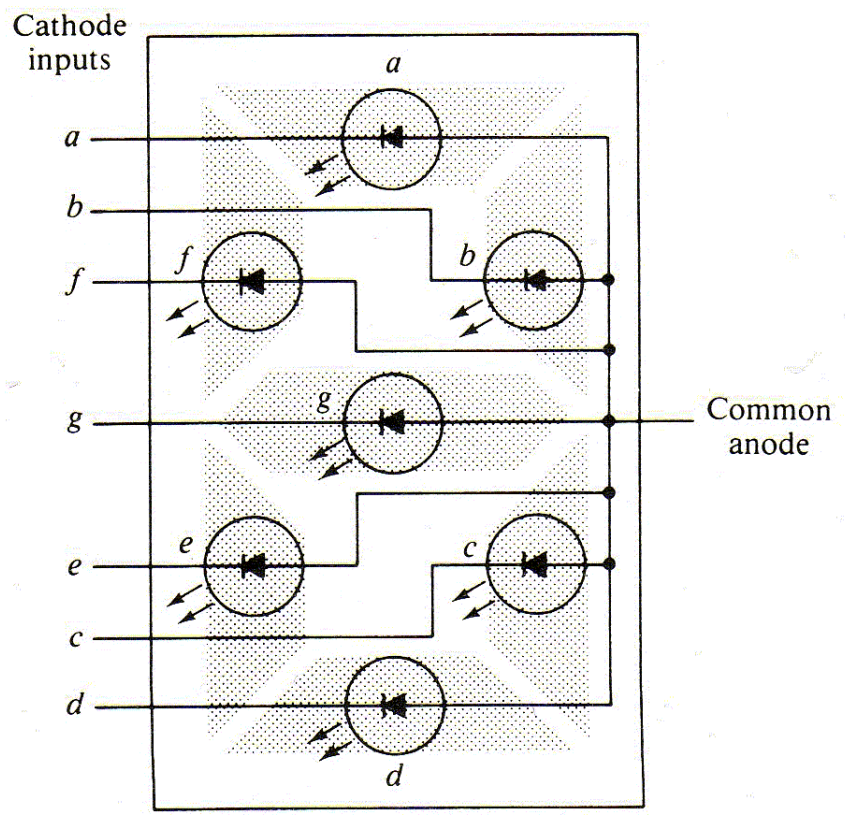


(b) Wiring of seven-segment LED display

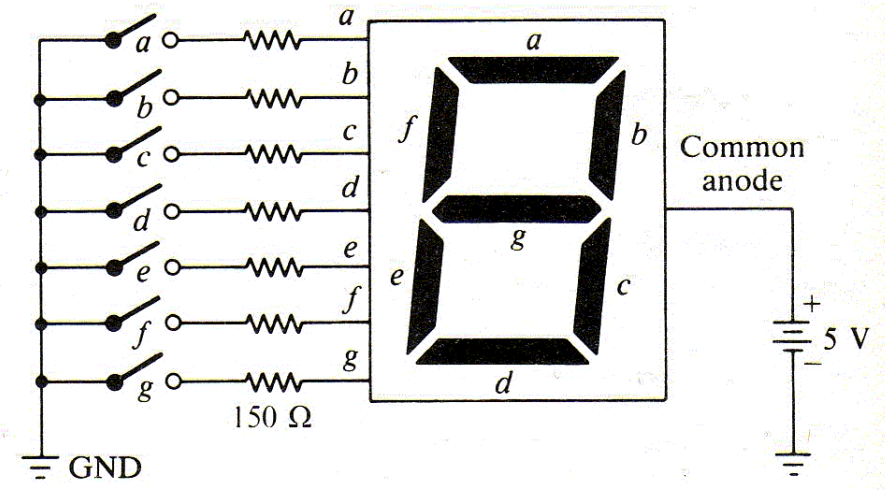

(c) Operating seven-segment LED display

Fig. 7-11

Seven Segment Display

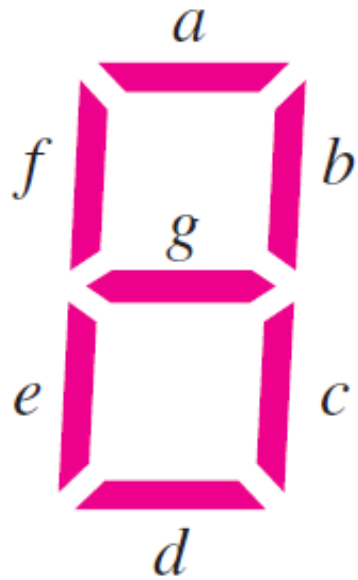

(a) Segment arrangement

(b) Formation of the ten digits
and certain letters



Binary coded decimal (BCD) number

- BCD means that each decimal digit, 0 through 9, is represented by a binary code of four bits.

Decimal/BCD conversion.


Decimal Digit	0	1	2	3	4	5	6	7	8	9
BCD	0000	0001	0010	0011	0100	0101	0110	0111	1000	1001

- Invalid Codes: 11-15

- 1010, 1011, 1100, 1101, 1110, and 1111




7-Segment Display Circuit Diagram

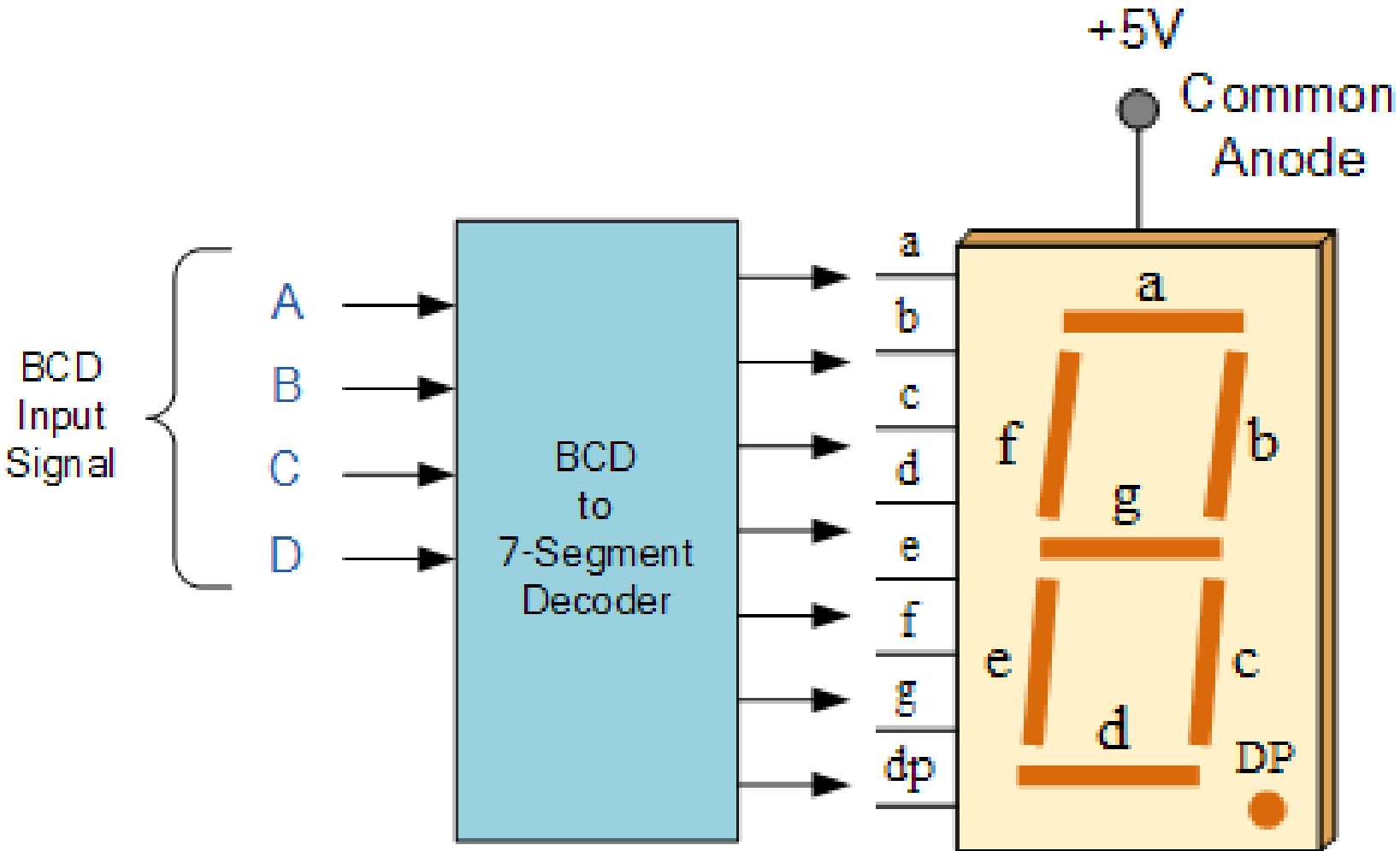



Decoder Truth Table

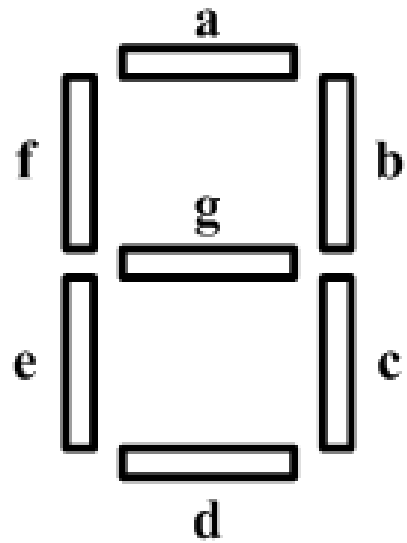

Decimal Digit	Input BCD	Seven-Segment Decoder Outputs						
		a	b	c	d	e	f	g
0	0 0 0 0	1	1	1	1	1	1	0
1	0 0 0 1	0	1	1	0	0	0	0
2	0 0 1 0	1	1	0	1	1	0	1
3	0 0 1 1	1	1	1	1	0	0	1
4	0 1 0 0	1	0	1	1	0	1	1
5	0 1 0 1	1	0	1	1	0	1	1
6	0 1 1 0	1	0	1	1	1	1	1
7	0 1 1 1	1	1	1	0	0	0	0
8	1 0 0 0	1	1	1	1	1	1	1
9	1 0 0 1	1	1	1	1	0	1	1
All other inputs		0	0	0	0	0	0	0



The Standard SOP Form

- A standard SOP expression is one in which **all the variables** in the domain appear in **each product term**
- Binary Representation:


$$A\bar{B}C\bar{D} = 1 \cdot \bar{0} \cdot 1 \cdot \bar{0} = 1 \cdot 1 \cdot 1 \cdot 1 = 1$$

Binary value: 1010



Constructing the Logic

Decimal Digit	Input BCD				Seven-Segment Decoder Outputs						
	a	b	c	d	e	f	g				
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	1	0	1	1	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1	0	1	1
All other inputs					0	0	0	0	0	0	0

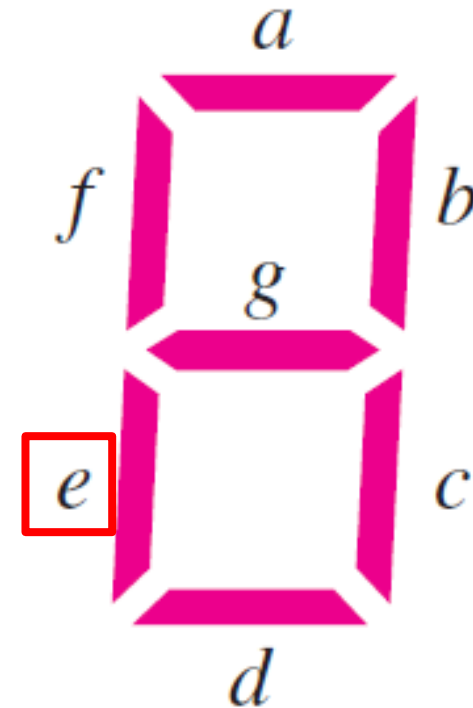

Standard SOP for e

$$e = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}C\overline{D} + \overline{A}B\overline{C}\overline{D} + A\overline{B}\overline{C}\overline{D}$$

0

2

6

8

8



Logic Simplification

$$\square a = A'C + A'BD + B'C'D' + AB'C'$$

$$\square b = A'B' + A'C'D' + A'CD + AB'C'$$

$$\square c = A'B + A'D + B'C'D' + AB'C'$$

$$\square d = A'CD' + A'B'C + B'C'D' + AB'C' + A'BC'D$$

$$\square e = A'CD' + B'C'D'$$


$$\square f = A'BC' + A'C'D' + A'BD' + AB'C'$$

$$\square g = A'CD' + A'B'C + A'BC' + AB'C'$$





Segment e Logic Circuit

BCD Inputs

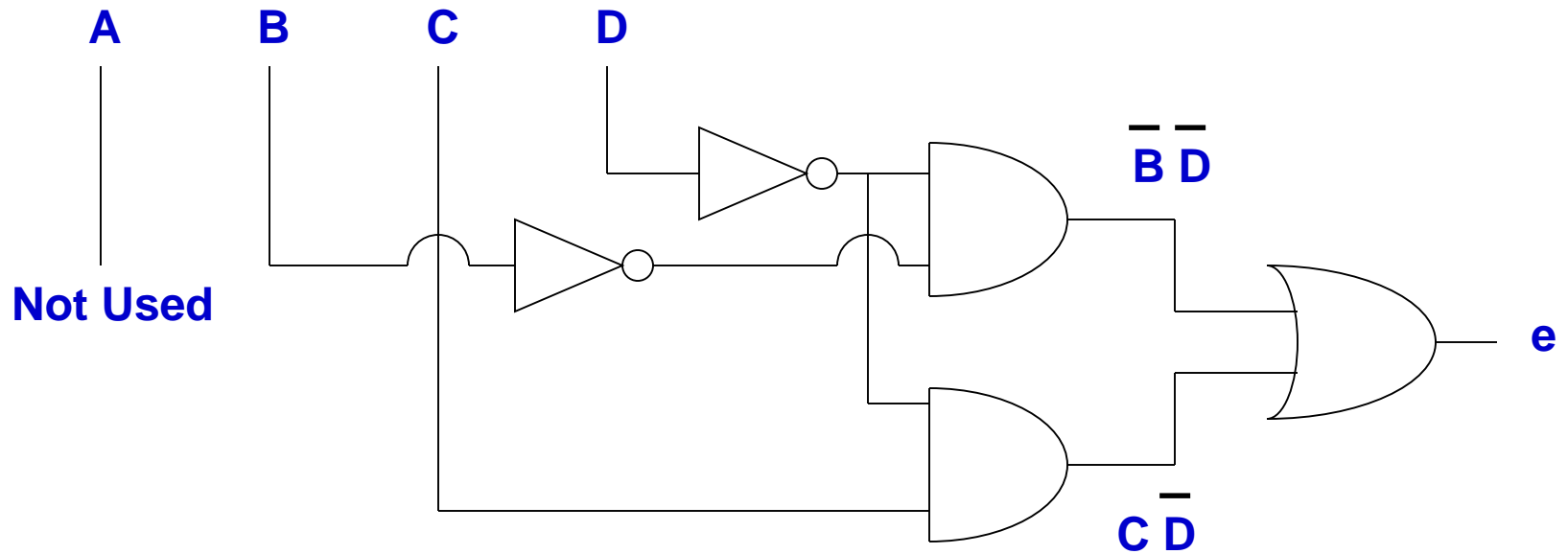



7-Segment Display used for Letter

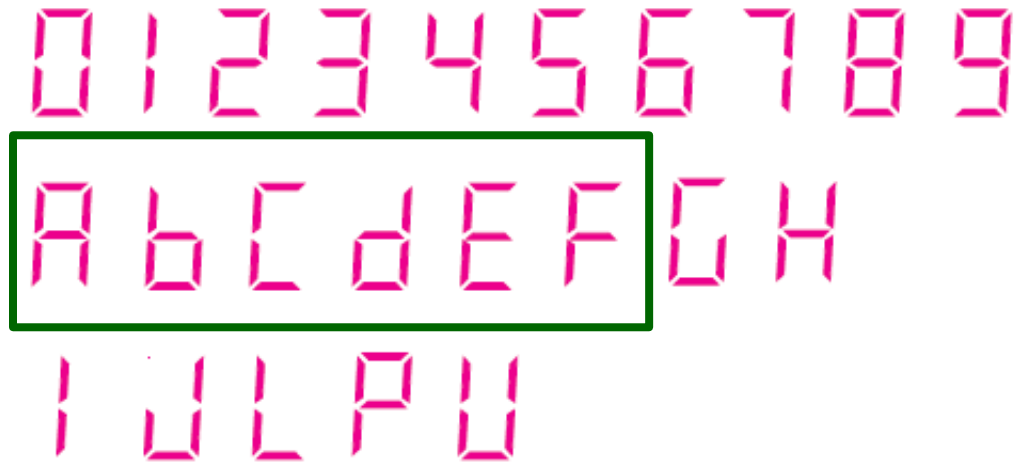
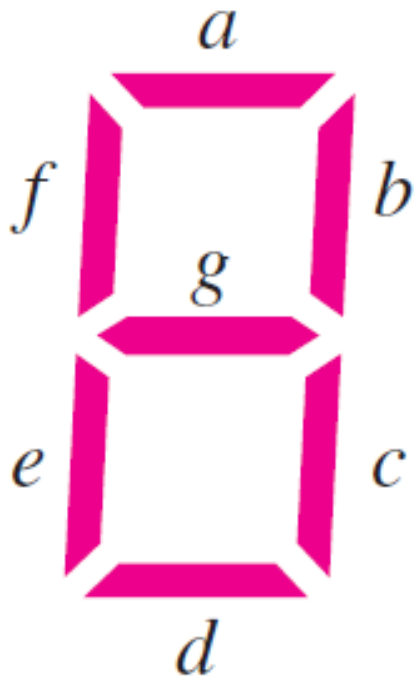


Active segments for each of the five letters used in the system display.

Letter	Segments Activated
A	<i>a, b, c, e, f, g</i>
b	<i>c, d, e, f, g</i>
C	<i>a, d, e, f</i>
d	<i>b, c, d, e, g</i>
E	<i>a, d, e, f, g</i>



7-Segment Display used for Letter

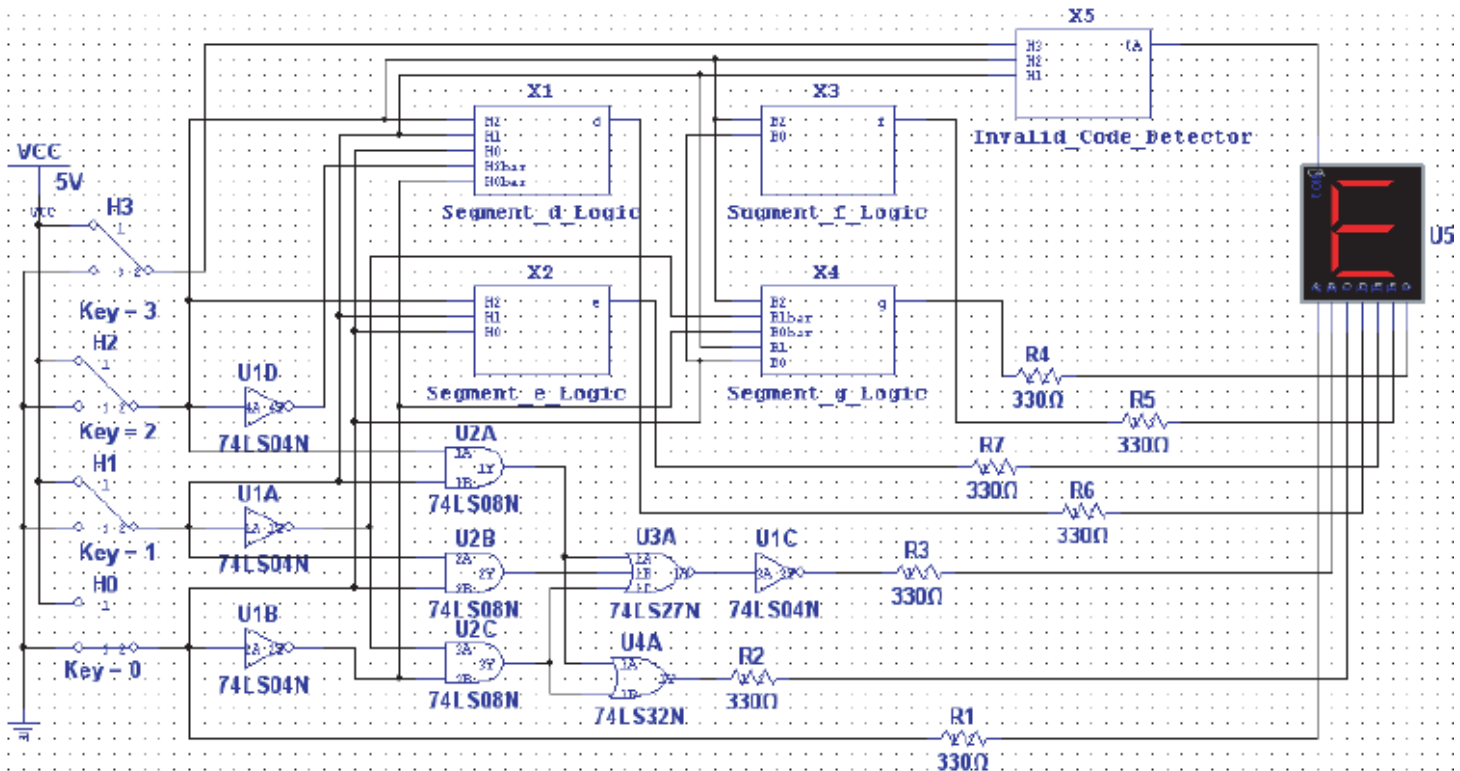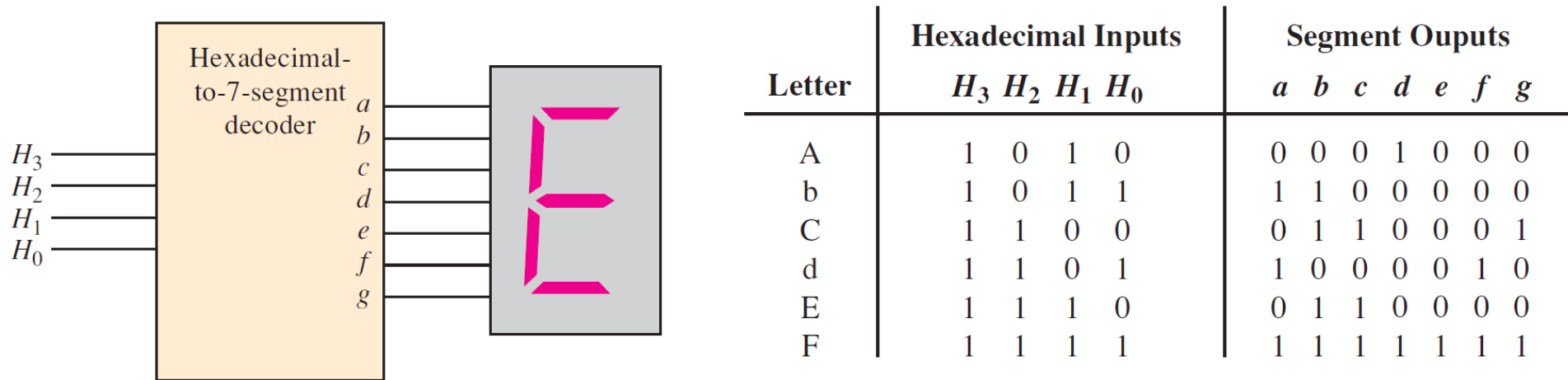



Example: Digital Clock

